

Class 10 Physics

Chapter 12 - Electricity

Activity 12.1

Objective: Construct an electric circuit to verify Ohm's law.

Materials Required: Resistor, ammeter, voltmeter, battery, wires.

Procedure: Connect ammeter in series, voltmeter in parallel across resistor. Turn on current.

Observation: Voltage increases proportionally with current.

Discussion: Current and voltage follow a linear relationship.